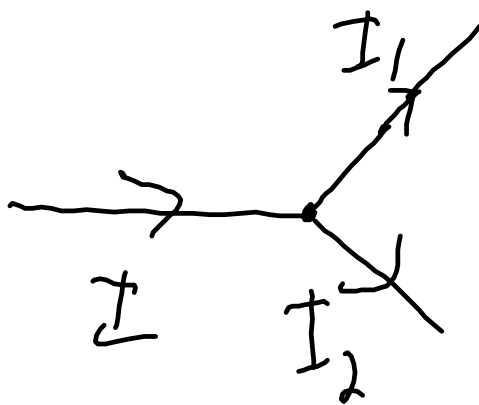


Kirchhoff's Laws

Laws for electric circuits

From conservation of charge we can derive a junction law




$$I = I_1 + I_2$$

KJL

Kirchhoff's Junction Law

Loop Law

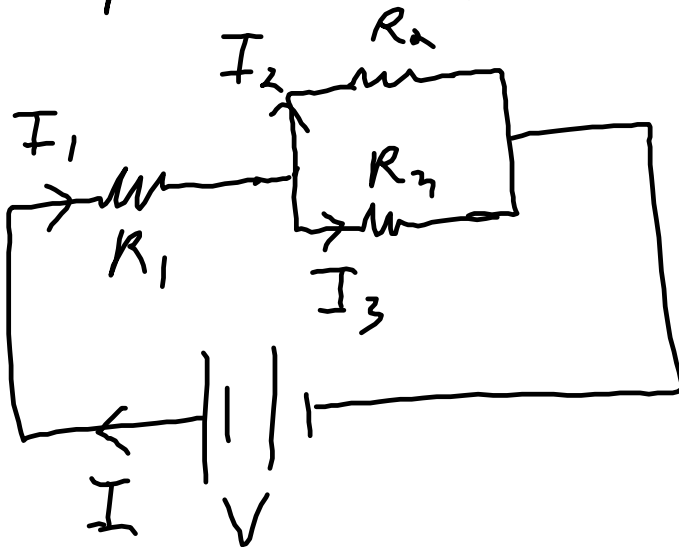

Conservation of energy

Power in = Power out
 ↑ battery ↑ resistors dissipating energy as heat

$$VI = I_1^2 R_1 + I_2^2 R_2 + I_3^2 R_3$$

or

$$V(I) = V_1(I) + V_2 I_2 + V_3 I_3$$

$$VI = V_1 I + V_2 I_2 + V_3 I_3$$

$$I = I_2 + I_3$$


so if $V_2 = V_3$

$$VI = V_1 I + (V_2 + V_3) I$$

$$\boxed{V = V_1 + V_2 + V_3}$$

loop Law voltages around

any loop add to zero.

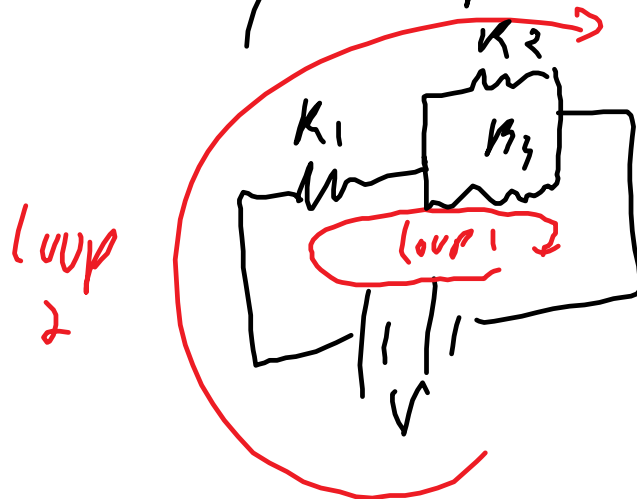

loop 1

$$V = V_1 + V_3$$

loop 2

$$V = V_1 + V_2$$

eg. in the above circuit, set

$$V = 6.0V \quad R_1 = 100\Omega$$

$$R_2 = 250\Omega \quad R_3 = 500\Omega$$

Determine a) R_T
b) I_1, I_2, I_3

c) V_1, V_2, V_3

d) which resistor dissipates most power?

what is the power output?

$$R_T = R_1 + R_2 \dots \text{Series}$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots \quad \text{Parallel}$$

$$= \frac{6.0V - 0.023A(100\Omega)}{250\Omega} = \frac{3.7V}{250\Omega}$$

$$I_2 = \boxed{0.0148 A}$$

$$I_3 = \frac{3.7V}{500\Omega} = \boxed{0.0074A}$$

$$V = 6V \quad V_1 = 2.3V \quad V_2 = V_3 = 3.7V$$

$$P_1 = I^2 R_1 = 0.023^2 \times 100$$

$$* \textcircled{P_2} = I^2 R_L = 0.014^2 (250)$$

Block 1-2

Electric Circuits and Kirchhoff's Laws


Q9 p 477

$$r = 1 \mu m$$

$$\rho = 10^{29} e^- / m^3$$



$$1r = ?$$

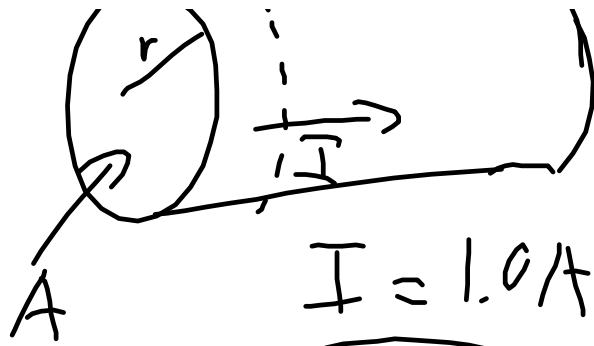

$$v = ?$$

$$I = \frac{\Delta q}{\Delta t} \quad \rho = \frac{q}{V}$$

$$I = \frac{\rho V}{\Delta t} \quad V = \pi r^2 \Delta L$$

$$I = \rho \pi r^2 \left(\frac{\Delta L}{\Delta t} \right)$$

$$I = \rho \pi r^2 v$$

$$v = \frac{1.0 \text{ A} \frac{\cancel{\text{C}}}{\text{s}}}{\frac{10^{29} \cancel{\text{e}}}{\text{m}^3} (3.14) (1.0 \times 10^{-3} \text{ m})^2 \frac{1.60 \times 10^{-19} \cancel{\text{e}}}{\text{C}}}$$

$$v = 2.0 \times 10^{-5} \text{ m/s}$$

Q 31


$$P_{in} = P_{out}$$

$$V_{+} = \frac{mc\Delta T}{t}$$


$$\frac{m}{t} = \frac{VI}{c\Delta T}$$

Electric Circuits

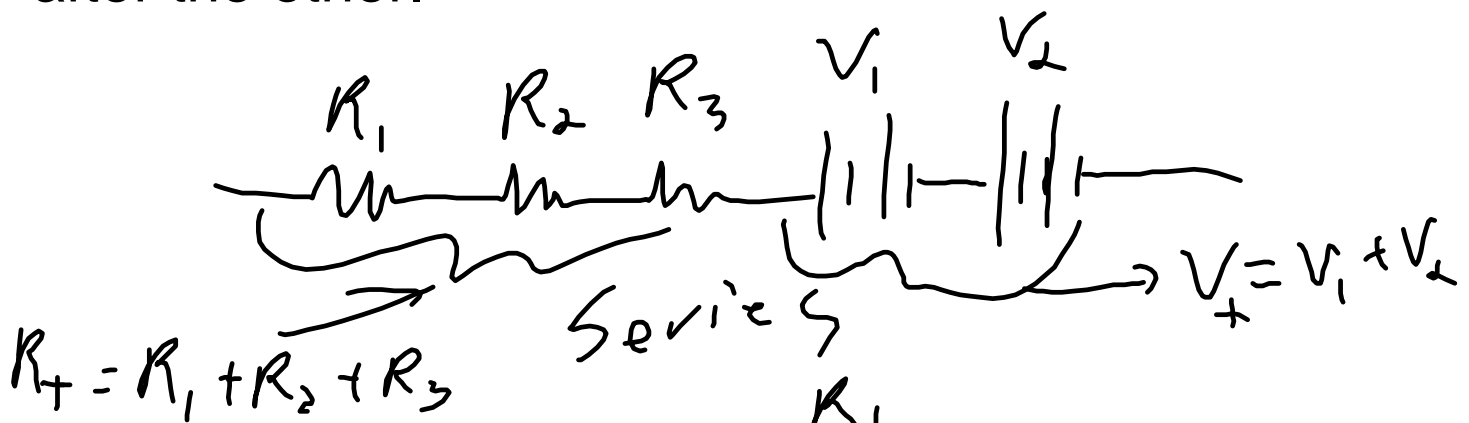Series circuit: circuits elements are one after the other.



Parallel

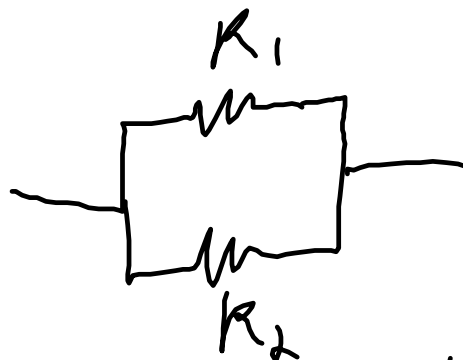

Equivalent resistance $\rightarrow \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$




$$V_- = V_1 = V_2$$



Law of conservation of charge - charge is not created or destroyed.

Kirchhoff's Junction

Law: I_1

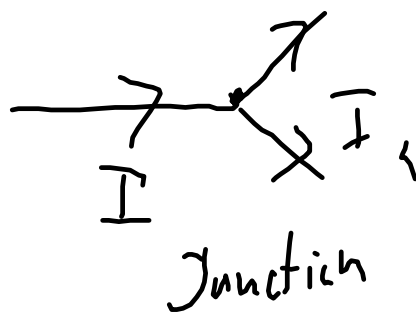

$$I = I_1 + I_2$$


$$V = IR$$



$$I = I_1 + I_2$$

$$\frac{V}{R_T} = \frac{V_1}{R_1} + \frac{V_2}{R_2}$$

$$V = V_1 = V_2$$

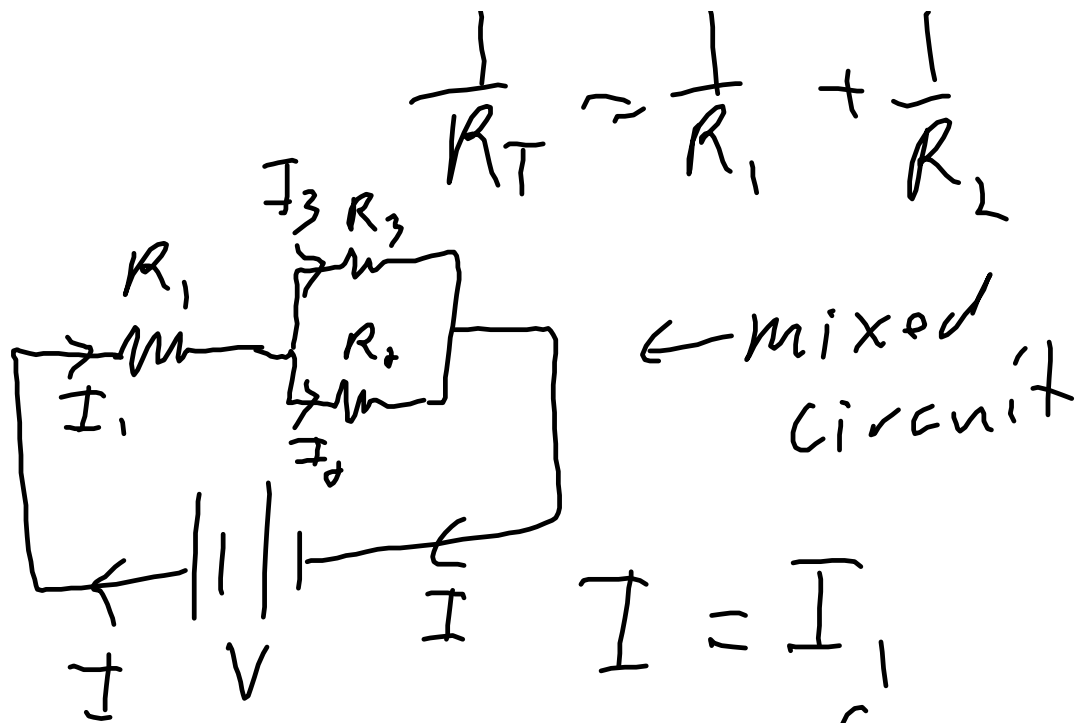

Law of Conservation of energy

$$P_{\text{input}} = P_{\text{output}}$$

↑ battery

↑ resistors
→ emit heat

$$VI = V_1 I_1 + V_2 I_2 + V_3 I_3$$

$$V_2 = V_3$$

$$I = I_2 + I_3$$

↑ $V_2 (I_2 + I_3)$


$$VI = V_1 I + V_2 I$$

$$V = V_1 + V_2 \quad \text{or}$$

$$V = V_1 + V_3$$

Kirchhoff's Loop Law

- Voltages around a loop add to zero.

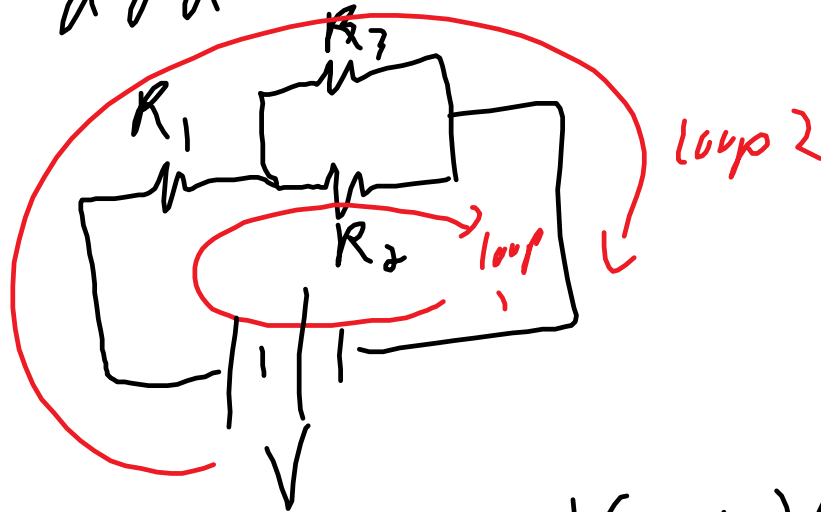

loop 1 $V = V_1 + V_2$

loop 2 $V = V_1 + V_3$

eg. In the above diagram
 Set $V = 6.0\text{V}$, $R_1 = 100\Omega$
 $R_2 = 250\Omega$ $R_3 = 500\Omega$
 Determine

a) equivalent resistance
- parallel resistors
- whole circuit

b) V_1, V_2, V_3

c) $(I), I_1, I_2, I_3$

$$\frac{1}{R_{T_2}} = \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{250} + \frac{1}{500}$$

$$\frac{1}{R_{T_2}} = \frac{3}{500} \quad R_{T_2} = 167 \Omega$$

$$R_T = R_1 + R_{T_2} = 100 + 167$$

Series

$R_T = 267 \Omega$

$$I = \frac{V}{R_T} = \frac{6.0V}{267\Omega} = 0.0225 \text{ A}$$

$$V_1 = IR_1 = 0.0225A \times 100\Omega$$

$$\boxed{V_1 = 2.25V}$$

Loop law $V = V_1 + V_2$

$$V_2 = V_3 = 6 - 2.25$$

$$\boxed{V_2 = V_3 = 3.75V}$$

$$I_1 = I$$

$$I_2 = \frac{V_2}{R_2} = \frac{3.75}{250} = 0.015A$$


$$\underline{I_3 = 0.0075A}$$

Which resistor gives off the most heat?


Electric Circuits and Kirchhoff's Laws

Resistor - dissipates electrical energy as heat, thus reducing the current for a particular voltage.

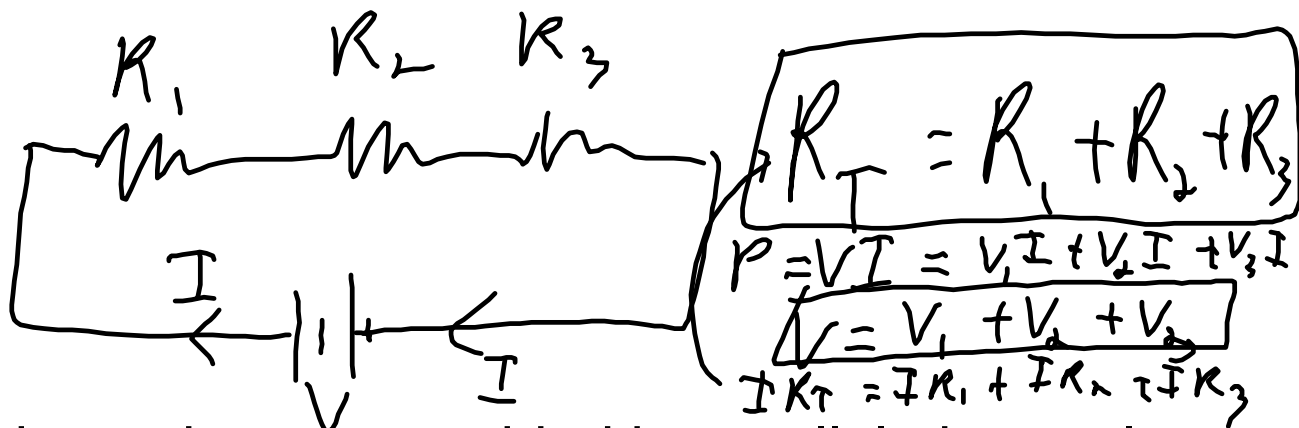If you add multiple resistors in series, the resistance of the circuit increases.



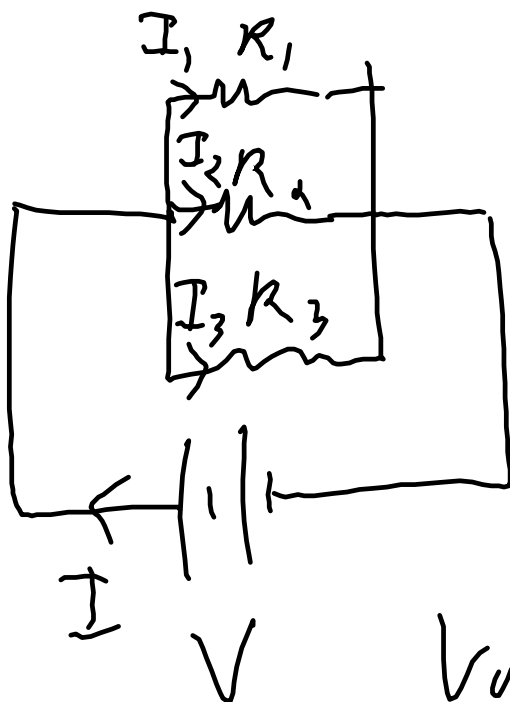If the resistors are added in parallel, the total resistance decreases.



Junction Law

$$I = I_1 + I_2 + I_3$$


$$\frac{V}{R_T} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$

Voltages in parallel are equal

$$V = V_1 = V_2 = V_3$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Mixed Circuit

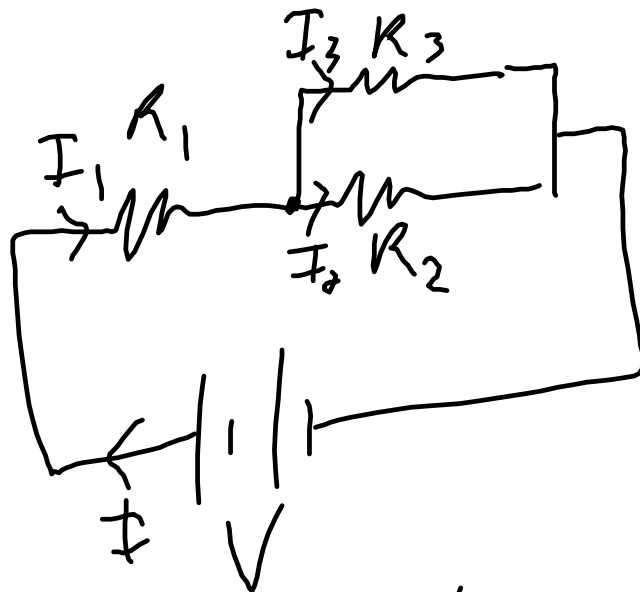

Kirchhoff's Loop Law

$$I = I_1 = I_2 + I_3$$

$$P_{in} = P_{out}$$

$$VI = V_1 I_1 + V_2 I_2 + V_3 I_3$$

$$V - V_1 - V_2 - V_3 = \underline{\underline{0}}$$

$$V_2 = V_3$$

$$VI = V_1 I + V_2 (I_2 + I_3)$$


$$VI = V_1 I + V_2 I$$


$$V = V_1 + V_2$$

$$\text{or } V = V_1 + V_3$$

Kirchhoff's Loop Law

- Voltages around a loop add to zero.

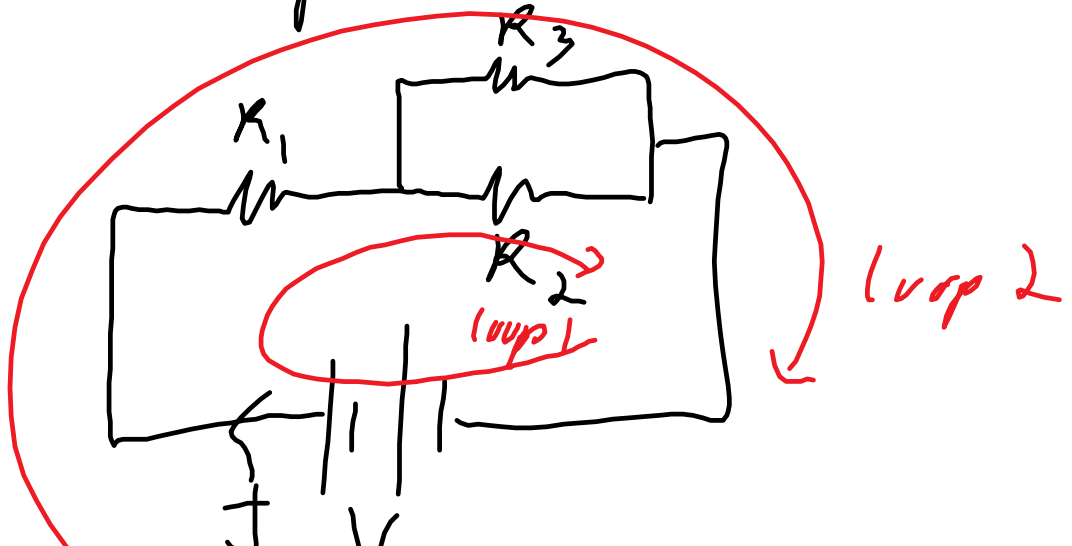

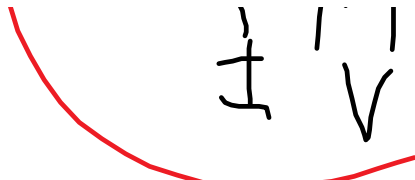

$V = V_1 + V_2$
 $V = V_1 + V_3$

loop 1
 loop 2

eg,

In the above circuit, the battery voltage is 6.0V, $R_1=100$ ohms, $R_2=250$ ohms and $R_3 = 500$ ohms.

Determine

- Equivalent resistance, R_T of the parallel section.
- Equivalent resistance, R_T of the whole circuit.
- Current out of the battery, I
- Voltage across R_1
- V and I of R_2 and R_3
- Which resistor gives off the most heat?

P498 Q1,2,3

P499 problems 1-11 odds